



# VCO Design Tips

Chuck Clark AF8Z  
July 25, 2009



# Lesson's Phase Noise Mode

$$L(f) = FkT/2P_o [1 + (f_o/2Q_L f)^2]$$

F=Active Device Noise Factor

k=Boltzmann's Constant

T=Temperature

P<sub>o</sub>=Output Power

F<sub>o</sub>=Oscillator Center Frequency

Q<sub>L</sub>=loaded resonator quality factor

f=frequency offset from carrier




# VCO Tips

Optimum Loaded to Unloaded Q  
 $2/3 Q_l/Q_o$  6 dB of resonator loss


This comes from solving Lessons eqn for the minimum of phase noise.

# One Approach to Higher

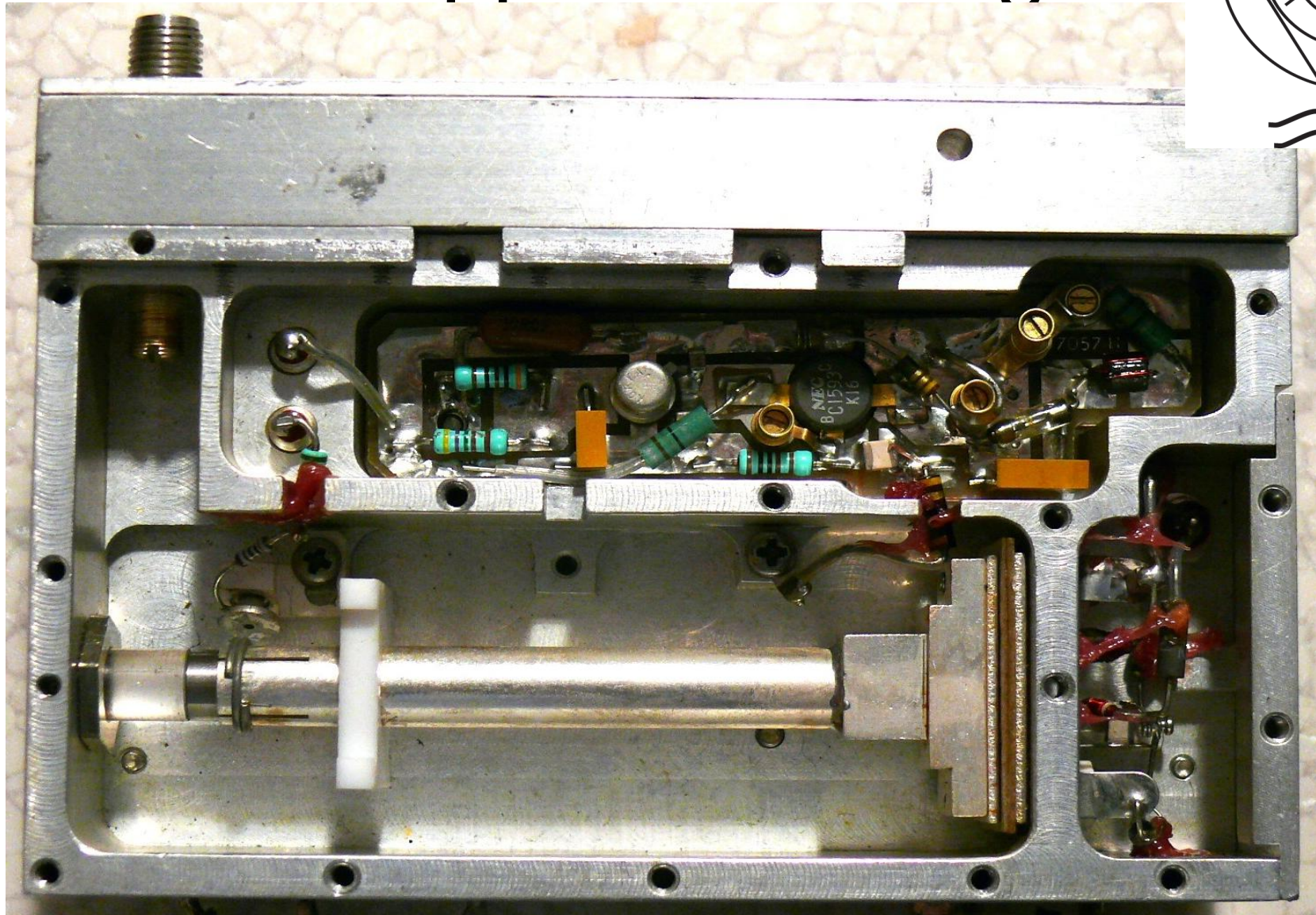



# Another

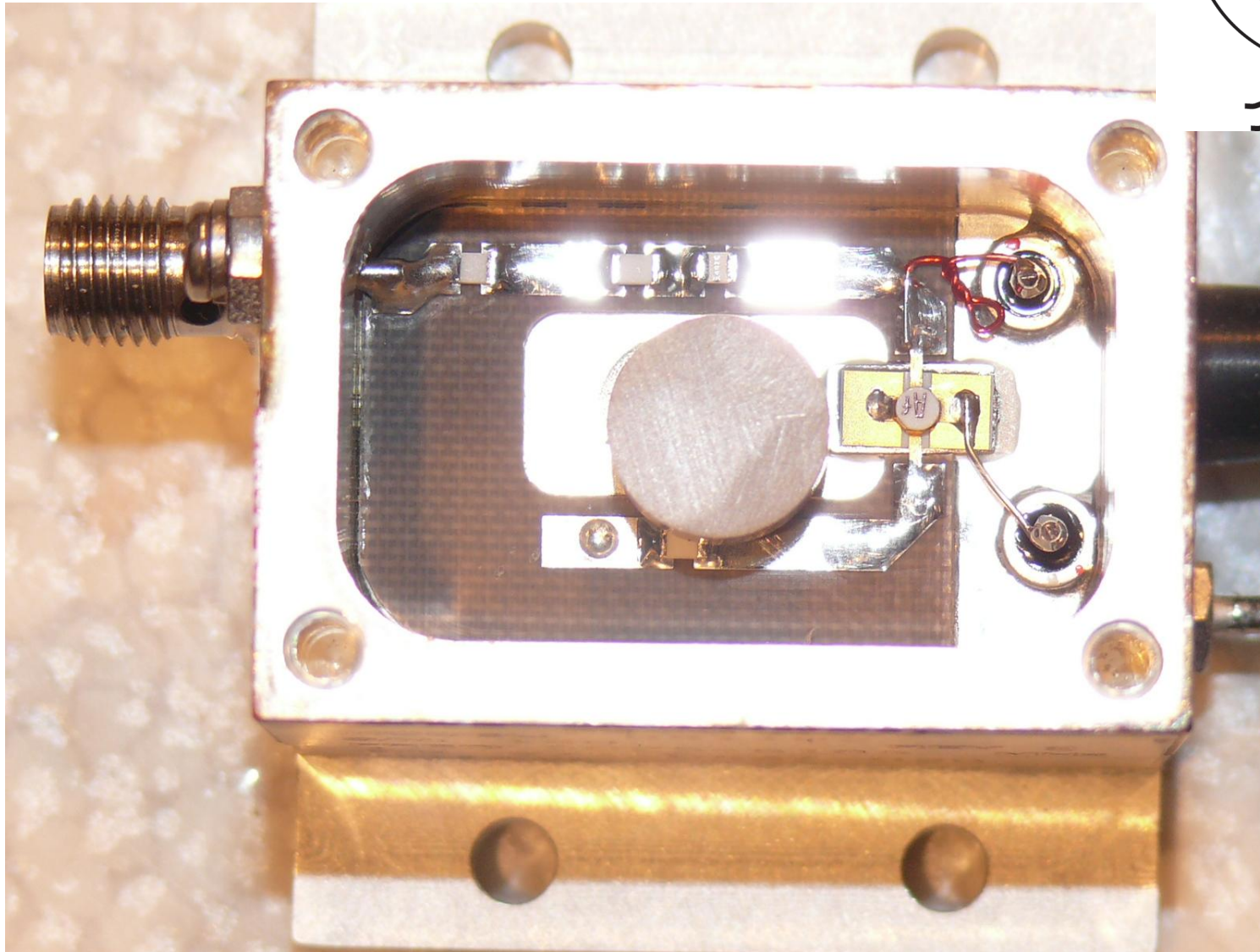



Q is purchased by the **CUBIC FOOT!**



# Amplifier

Run a large DC current.

Servo the DC current

Small device capacitances

High FT Oscillator Transistor

NEC 85633 is excellent below 1200 MHz


NEC 68133 above

Infineon and NXP also make good parts

# 1/f Noise Feedback, Servo the current



Clapp VCO with Noise Feedback

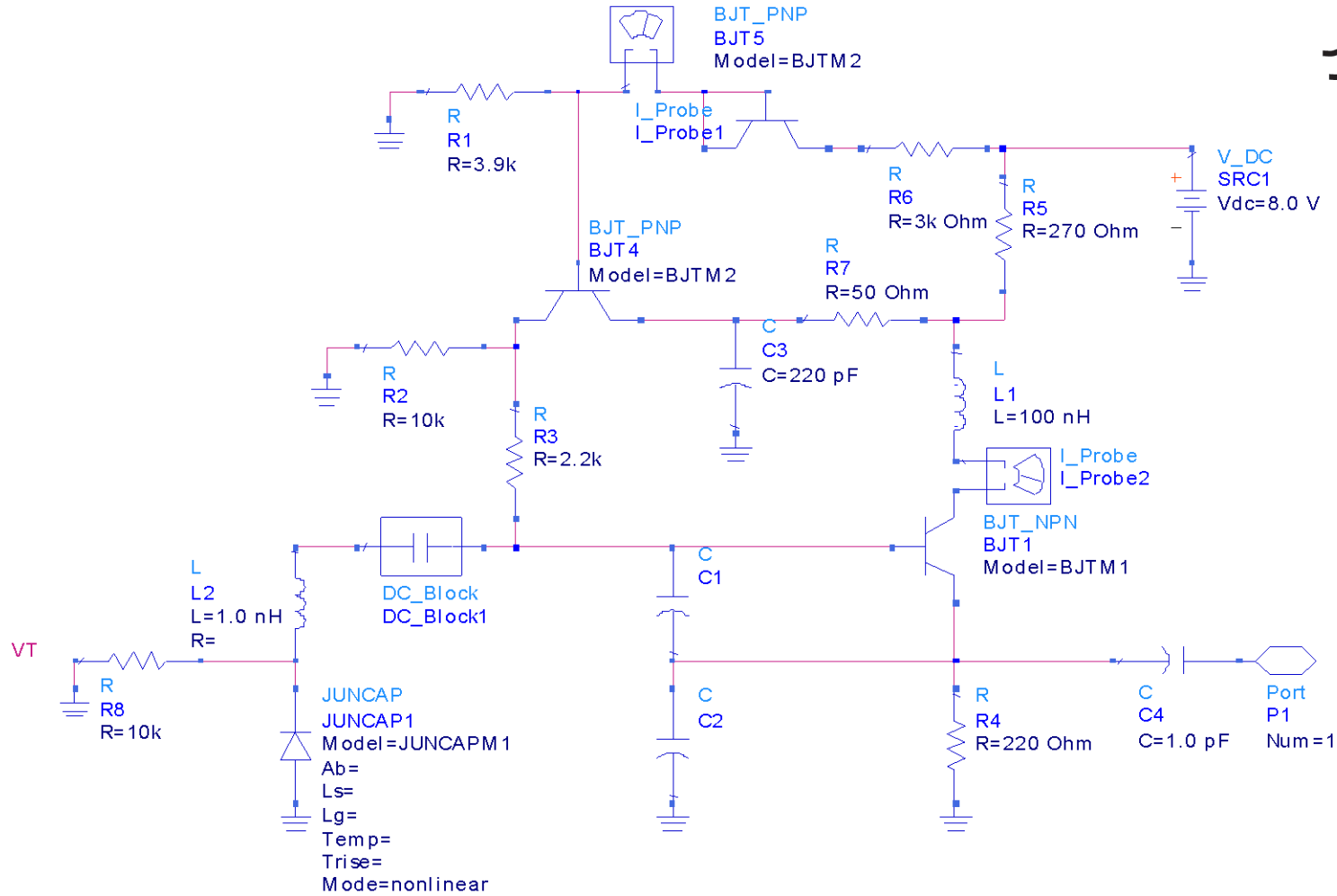





# Active Bias Circuit

PNP Transistor BC847

Beta =800

Low Noise

Suppresses gain of the RF transistor up to ~100 MHz.


Works the same as the feedback in a PLL

Can extend the noise improvement above the corner frequency of the PLL which is dictated by the reference frequency.




# Phase Noise of PLL

Loop Reduction of VCO Phase Noise

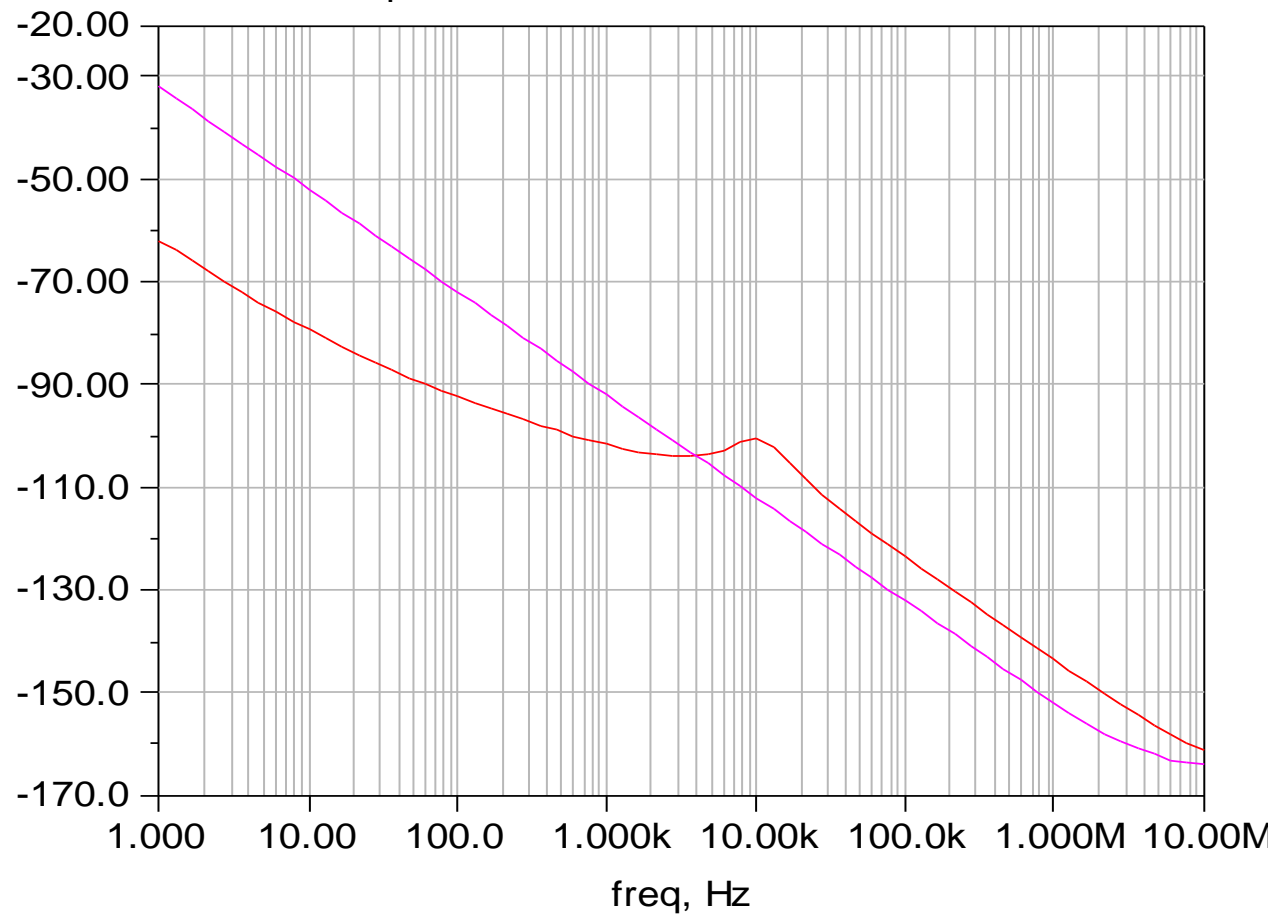



# Its all about Loop Gain

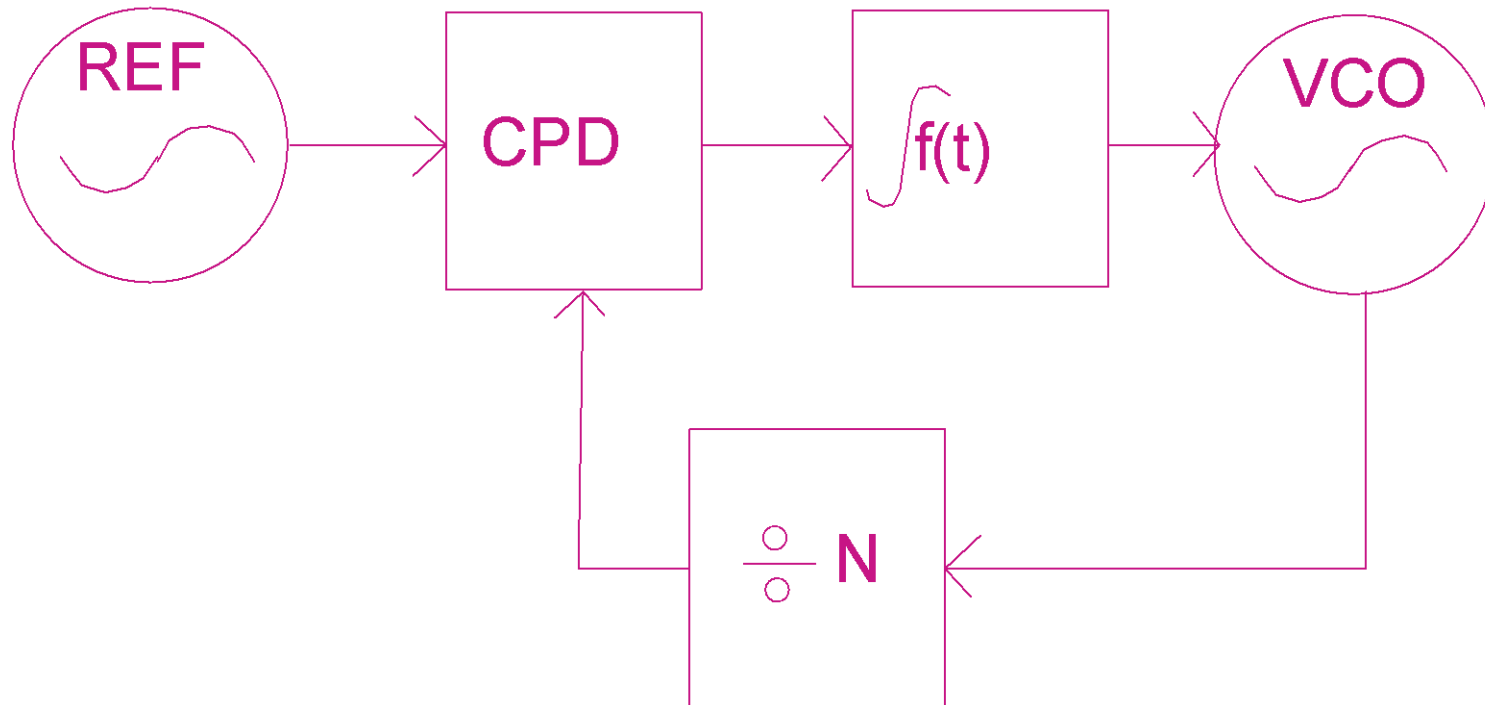



# Loop Transfer Function

$$B(s) = (K_d * F(s) * K_o) / (N * s)$$

$K_d$  = Phase Detector gain constant


$K_o/s$  = VCO gain, MHz/Volt

$F(s)$  = loop filter response

$N$  = loop divider ratio

$s$  = Heaviside operator,  $2 * \pi * f$

# Passive Filter

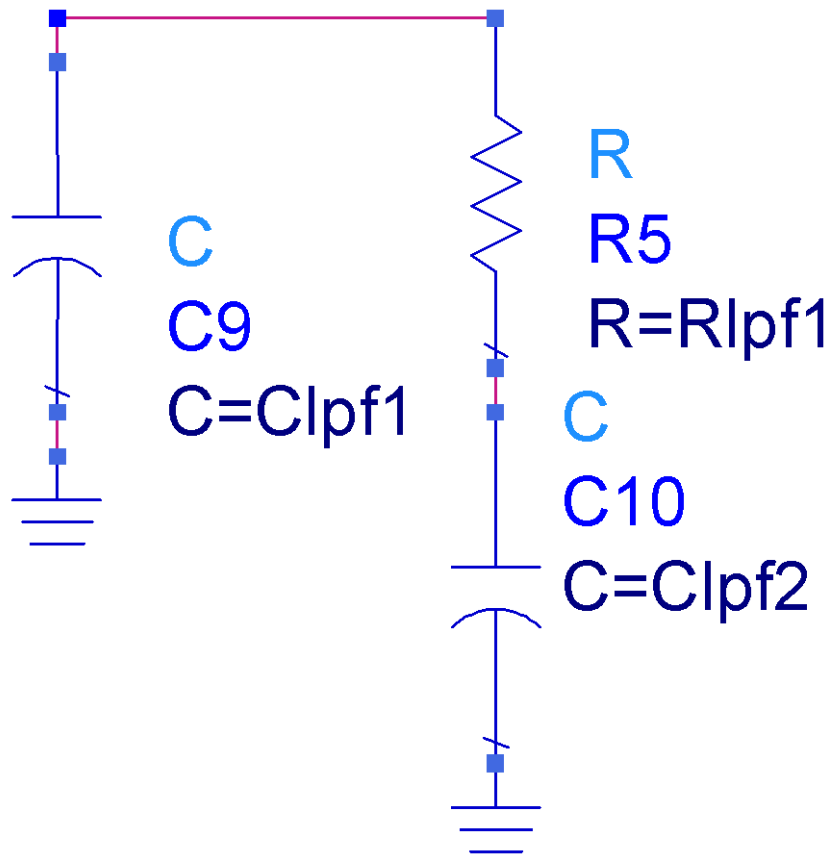


- Low Frequency Gain  $\sim 1$
- Other Passive filters possible.






# Loop Filter Gain

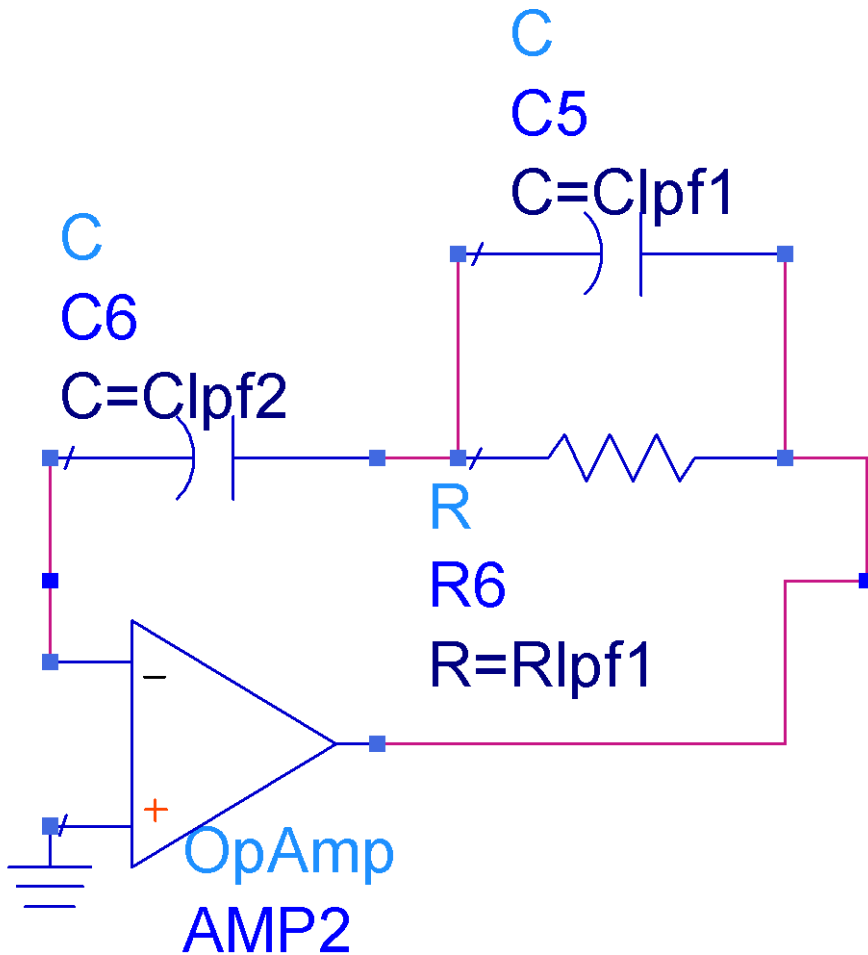

- Low Frequency Gain  $\sim \infty$




## Phase Noise vs Reference Frequency

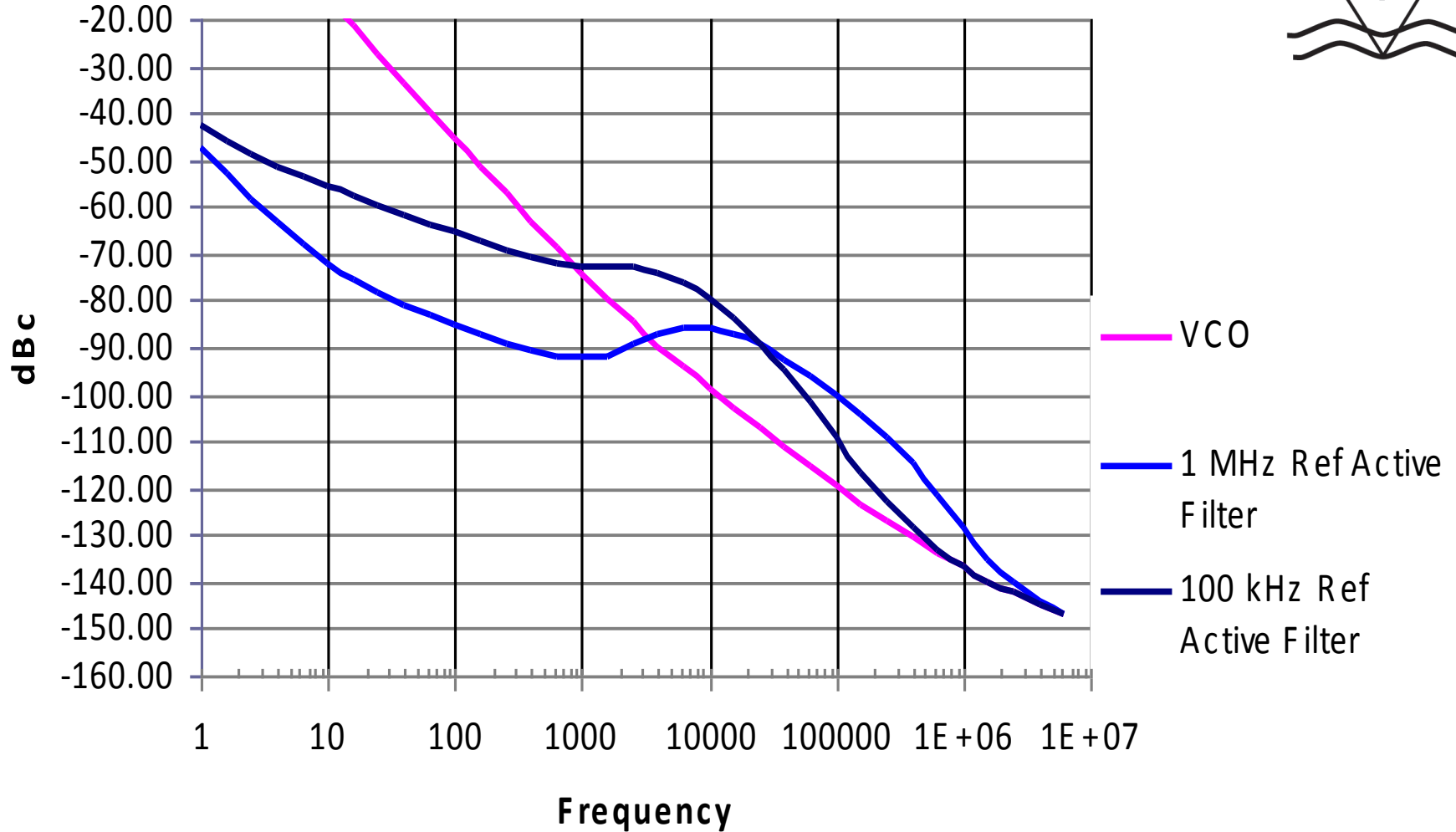




# Other Sources of Phase Noise

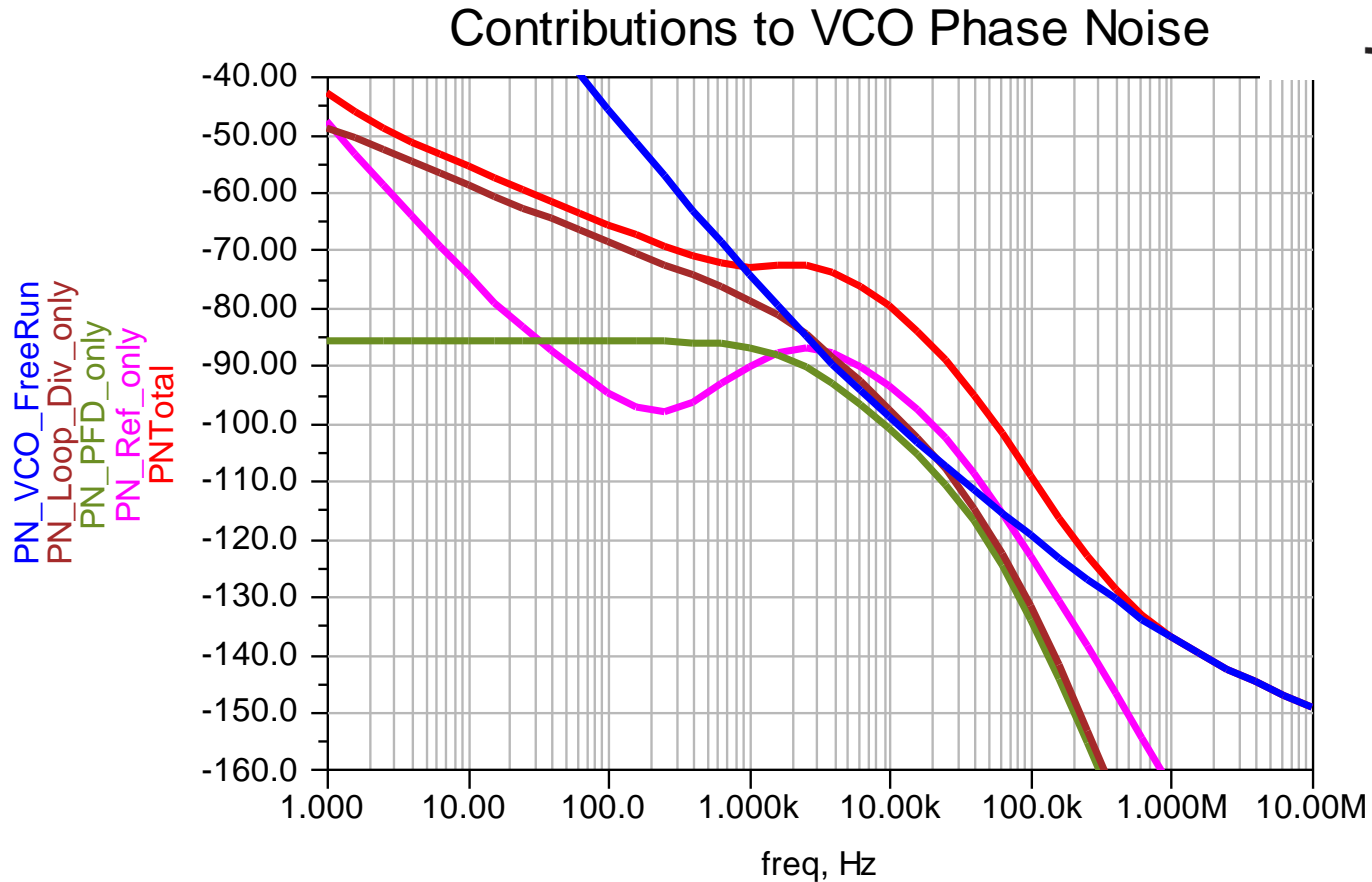



# 1 MHz Reference

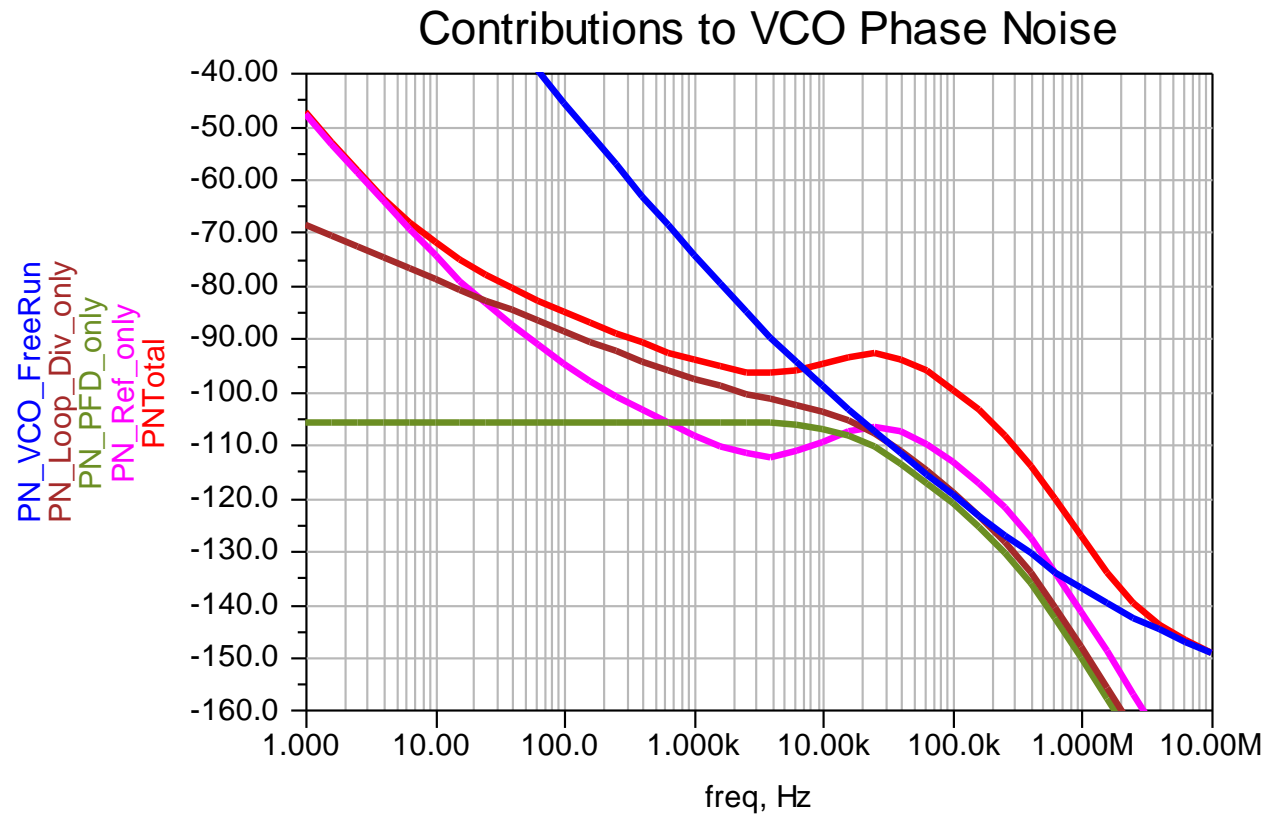

# Does the Reference Matter?




If other components limit the total noise....no.

If its noisy. Heck yes.

The application also matters.




# Clean vs Poor Reference Osc

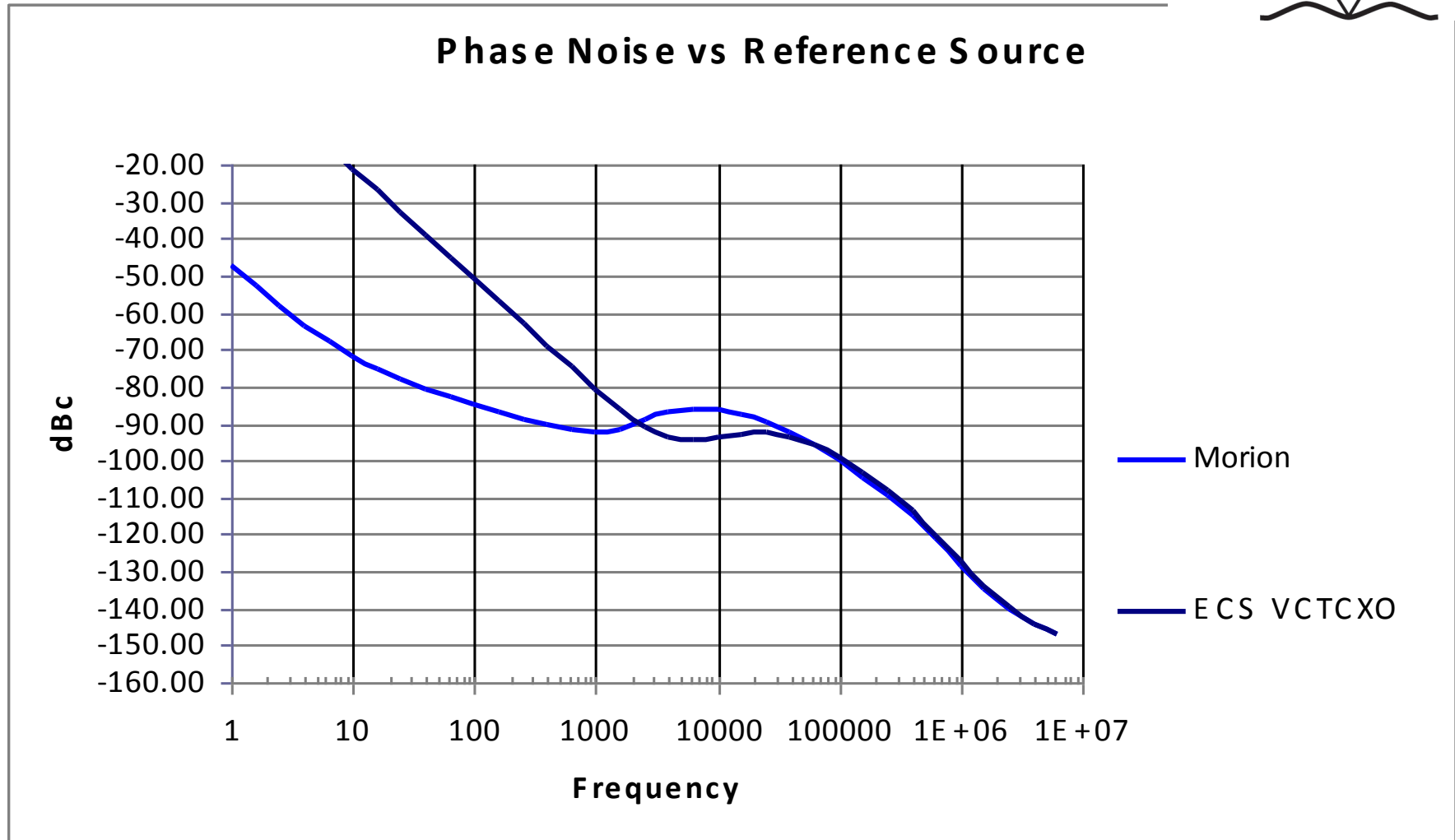




# Some Reference Oscillators

## Oscillator Phase Noise Comparison

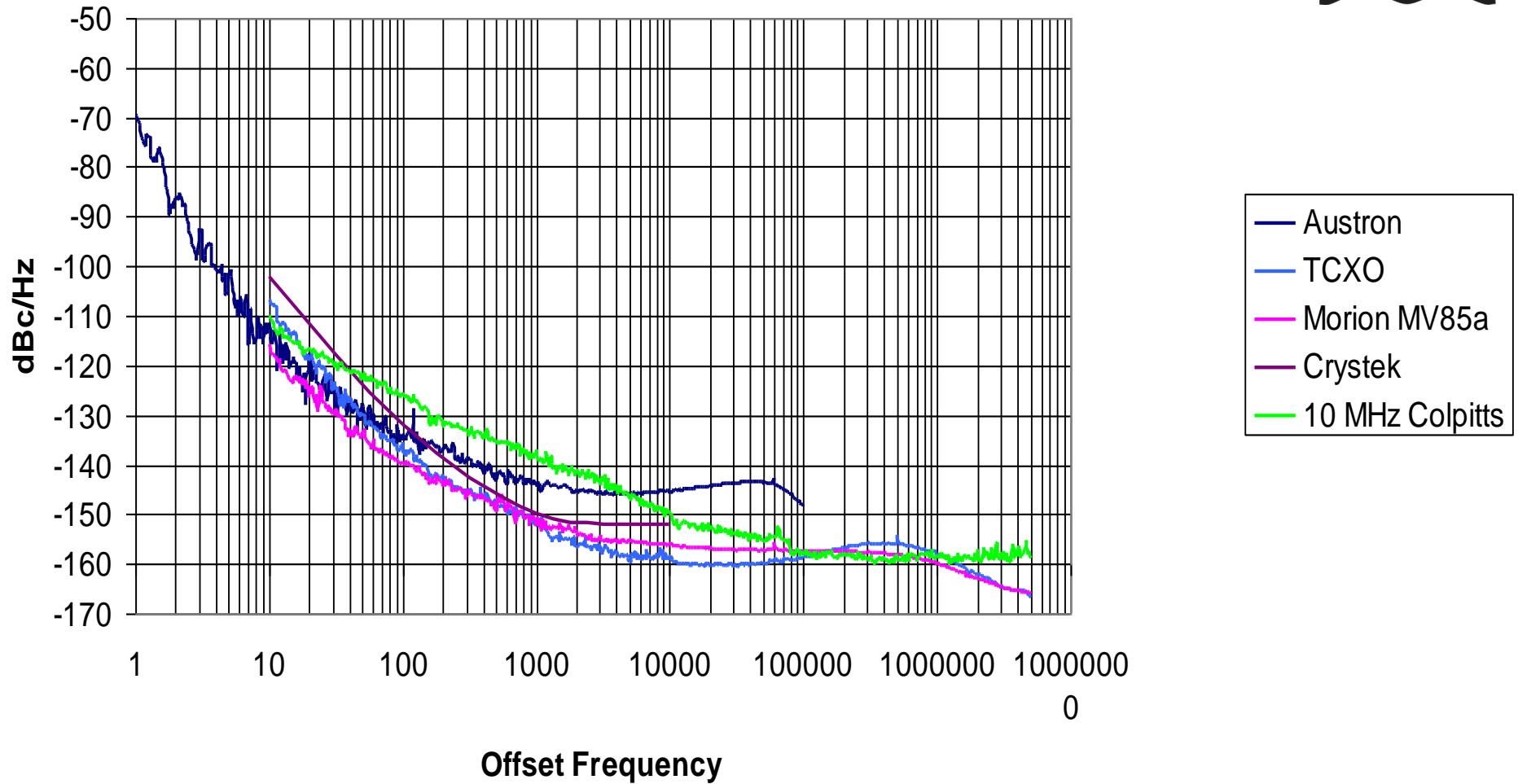



# What is that Stuff???

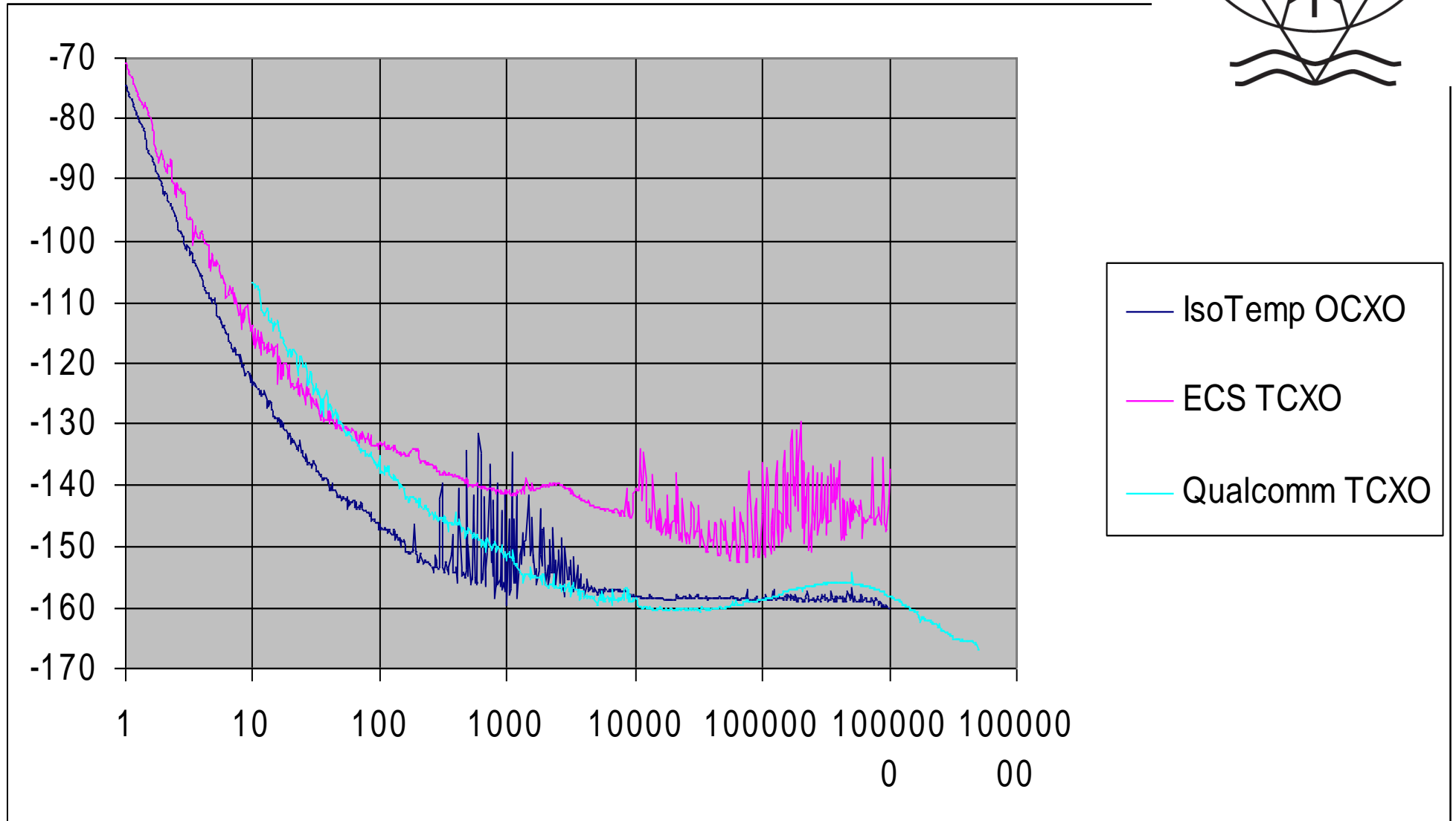



# Summary

Get all the Q you can.

Use a good oscillator transistor

Servo the current to reduce noise in the VCO  
below 100 MHz

Select the loop filter based on your application.

Select as high a reference frequency as possible

Find a clean reference.

# References



Fundamentals of RF Circuit Design with Low Noise Oscillators. Jeremy Everard

Copyright © 2001 John Wiley & Sons Ltd

ISBNs: 0-471-49793-2 (Hardback); 0-470-84175-3 (Electronic)

Noise in High-Frequency Circuits and Oscillators, Schiek, Rolfes, Siweris, 2006 John Wiley & Sons. ISBN 0-471-70607-6

The Design of Modern Microwave Oscillators for Wireless Applications, Rohde, Podar and Bock, 2005 John Wiley and Sons. ISBN 0-471-72342-8

ADS for simulation, by Agilent.

ADIsimPLL free from Analog Devices, [www.ADI.com](http://www.ADI.com)

<http://www.analog.com/en/rfif-components/pll-synthesizersvcos/products/index.html>

VCO data from Synergy Microwave, [www.synergy.com](http://www.synergy.com) DCMO80210-10